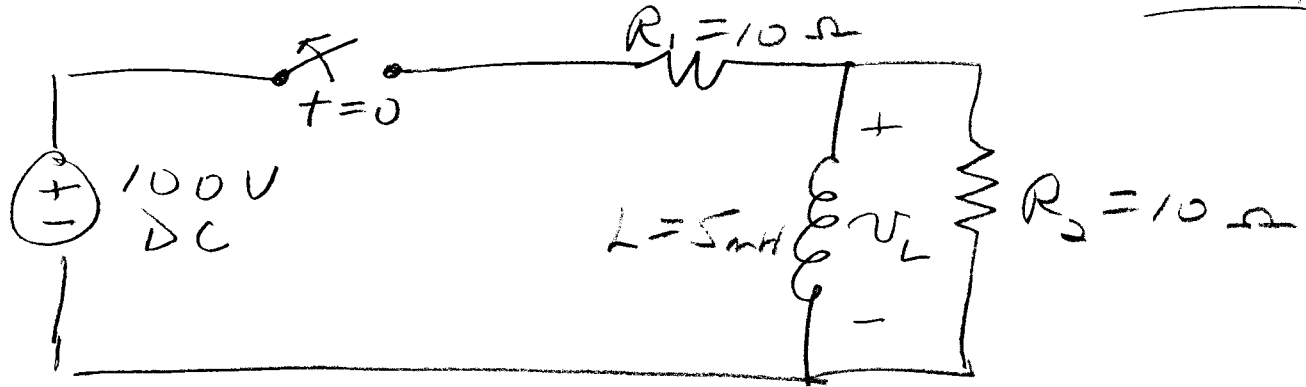



ECE 587 - OLD EXAM

FIRST-ORDER RL TRANSIENT EXAMPLE. FIND $V_L(t)$



BEFORE SWITCHING ACTION, IN STEADY-STATE, INDUCTOR LOOKS LIKE A SHORT CIRCUIT


$t < 0$

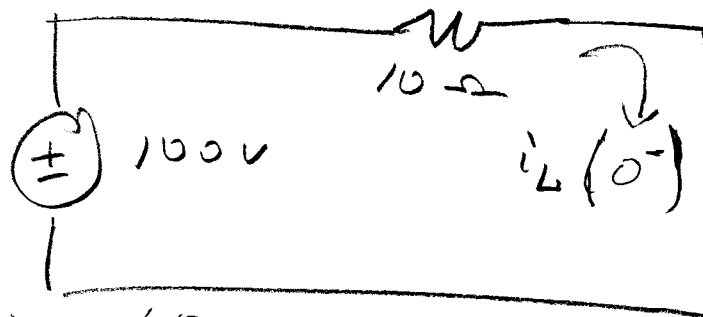

NOTE R_2 SHORTED OUT, HAS NO CURRENT

$$\text{SO } i_L(0^-) = \frac{100\text{V}}{10\Omega} = 10\text{A}$$

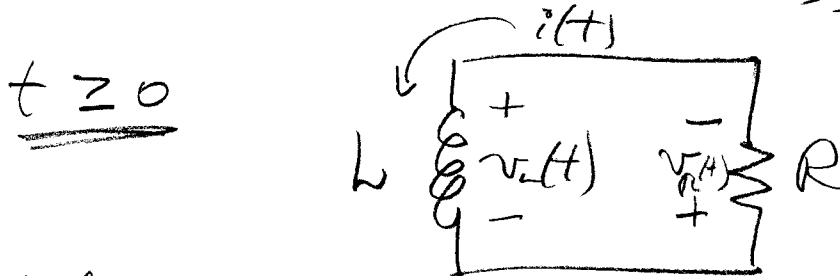AFTER SWITCHING OCCURS, HAVE THIS CIRCUIT



WHERE

$$i(t=0) = i(0^-) = 10\text{A}$$

WRITING ODE

$$L \frac{di(t)}{dt} + R i(t) = 0$$

IN STEADY-STATE $i_{ss}(t) = 0$ SINCE THERE IS NO SOURCE

FOR TRANSIENT PORTION OF SOLUTION, CHARACTERISTIC EQUATION FOUND FROM

$$L s I(s) + R I(s) = 0 = (Ls + R) I(s) = 0$$

OR $(Ls + R) = 0$ WHERE $i_{tr}(t) = A e^{st} = A e^{-\frac{R}{L}t}$

RL FIRST-ORDER (CONT.)

TOTAL SOLUTION $i(t) = i_{ss}(t) + i_{tr}(t) = A e^{-R/L t} + \geq 0$ At $t=0$ $i(0) = A e^0 = A = 10 \text{ A}$; $\frac{R}{L} = \frac{10}{0.005} = 2000$

$$\Rightarrow i(t) = 10 e^{-2000t} \text{ A } t \geq 0$$

$$v_L(t) = L \frac{di_L(t)}{dt} = L [10(-2000) e^{-2000t}] \text{ V}$$


$$= -100 e^{-2000t} \text{ V, } t \geq 0$$

SO VOLTAGE
DECAYS FROM
-100 TO 0.

NOTE BEFORE SWITCHING ACTION $v_L(0^-) = 0 \text{ V}$.

At $t=0$, $v_L(0) = -100 \text{ V}$. BUT THIS IS OK SINCE
VOLTAGE ACROSS INDUCTOR CAN CHANGE
INSTANTANEOUSLY.

GREENWOOD 2.3

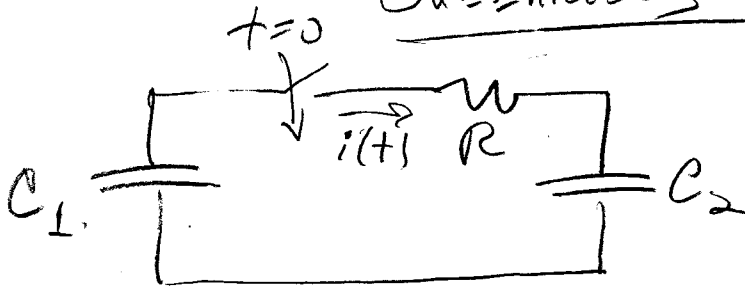

$$R = 5 \Omega$$

$$C_1 = 60 \mu F$$

$$C_2 = 40 \mu F$$

$$Q_{C_1}(0) = 1 C; Q_{C_2}(0) = 0$$

$$Q = CV \Rightarrow V_{C_1}(0) = \frac{1}{60 \mu F} = \underline{16.667 V}$$

$$V_{C_2}(0) = 0 V$$

WRITING KVL
$$+\frac{1}{C_1} \int i dt + V_{C_1}(0) + Ri + \frac{1}{C_2} \int i dt + V_{C_2}(0) = 0$$

TAKING

DERIVATIVE OF BOTH SIDES
$$\frac{d}{dt} \left(+\frac{1}{C_1} \int i dt + V_{C_1}(0) + Ri + \frac{1}{C_2} \int i dt + V_{C_2}(0) = 0 \right)$$

$$+\frac{1}{C_1} i + R \frac{di}{dt} + \frac{1}{C_2} i = 0$$

$$\frac{di}{dt} + \frac{1}{RC_{eq}} i = 0 \quad \text{WHERE } C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$

CHAR EQU.

$$s + \frac{1}{RC_{eq}} \Rightarrow s = -\frac{1}{RC_{eq}}; C_{eq} = 24 \mu F$$

$$\frac{1}{RC_{eq}} = 8333$$

IN STEADY-STATE $i_{ss}(t) = 0$ SO

$$i(t) = i_{tr}(t) = A e^{-\frac{t}{RC_{eq}}} \quad t \geq 0$$

AT $t=0$, SINCE CAPACITOR VOLTAGE CANNOT CHANGE INSTANTANEOUSLY

$$i(0) = \frac{16.667 - 0}{5} = 3.333 A$$

SO APPLYING INITIAL CONDITION

$$i(0) = 3.333 = A e^{-\frac{0}{RC_{eq}}} = A \Rightarrow A = 3.333$$

$$i(t) = 3333 e^{-8333t} A \quad t \geq 0$$

(a) PEAK CURRENT = 3.333 A

(b) $i(200 \mu s) = \underline{629.6 A}$

$$\begin{aligned}
 (c.) \quad v_{c2}(t) &= \frac{1}{C_2} \int_0^t i \, dt + v_{c2}(0) \\
 &= \frac{1}{C_2} 3333 \left. \frac{1}{-8333} e^{-8333t} \right|_0^t + 0 \\
 &= -10,000 e^{-8333t} + 10,000 + 0
 \end{aligned}$$

$$\text{As } t \rightarrow \infty \Rightarrow v_{c2}(\infty) = \underline{10,000V}$$

$$E = \frac{1}{2} C_2 v^2 = \frac{1}{2} (40 \times 10^{-6}) (10,000)^2 = \underline{2000 \text{ Joules}}$$

$$\begin{aligned}
 (d.) \quad v_{c1}(t) &= \frac{1}{C_1} \int_0^t (-i) \, dt + v_{c1}(0) \\
 &= \frac{1}{C_1} (-3333) \left. \frac{1}{-8333} e^{-8333t} \right|_0^t + 16,667 \\
 &= 6,666 e^{-8333t} - 6,666 + 16,667
 \end{aligned}$$

$$\text{As } t \rightarrow \infty \quad v_{c1}(\infty) \neq \underline{10,000V}$$

NOTE IN EQUILIBRIUM, CAPACITORS HAVE SAME VOLTAGE.

$$\begin{aligned}
 \text{INITIAL ENERGY IN } C_1 &\text{ IS } \frac{1}{2} (60 \times 10^{-6}) (16,667)^2 \\
 &= 8333 \text{ Joules}
 \end{aligned}$$

$$\begin{aligned}
 \text{FINAL ENERGY IN } C_1 &\text{ IS } \frac{1}{2} (60 \times 10^{-6}) (10,000)^2 \\
 &= 3000 \text{ Joules}
 \end{aligned}$$

RESISTOR
DISSIPATES

$$8333 - (2000 + 3000) = \underline{3,333 \text{ J.}}$$