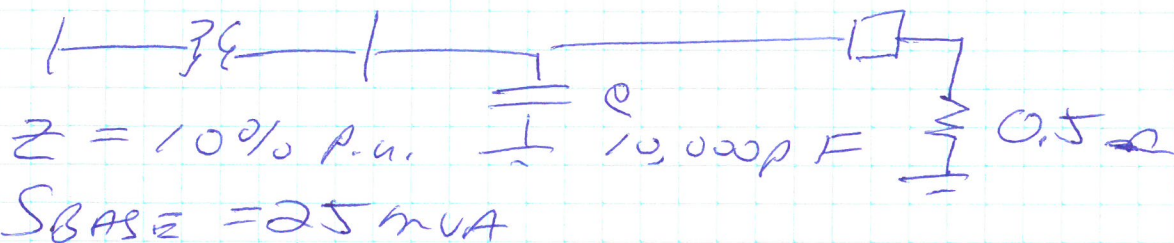


69 kV

12.47 kV



Assume CB clears the fault at current zero. Find TRV and peak stress.

$$Z_{\text{BASE}} = \frac{(V_{\text{BASE, LINE}})^2}{S_{\text{BASE}}} = \frac{(12.47)^2}{25} = 6.22 \Omega$$

$$R = 0 \Rightarrow L = \frac{X}{\omega} = \frac{0.1 \times 6.22}{377} = 1.65 \times 10^{-3} \text{ H} = 1.65 \text{ mH}$$

$$\tilde{I}_f = \frac{\tilde{V}_s}{R_{\text{fault}} + j\omega L} = \frac{\frac{12.47}{\sqrt{3}} \angle \theta}{0.5 + j0.622} = \frac{9.02 \text{ kA} \angle -51.2^\circ}{\text{RMS}}$$

$$v_s(t) = \frac{\sqrt{2} (12.470)}{\sqrt{3}} \cos(377t + \theta)$$

$$i_f(t) = \sqrt{2} 9.020 \cos(377t + \theta - 51.2^\circ)$$


Find θ , $i_f(t=0) = 0$ $377t + \theta - 51.2^\circ = \frac{\pi}{2}, \frac{3\pi}{2}$

$$\theta = \frac{\pi}{2} + 51.2^\circ$$

$$v_s(\theta = \frac{\pi}{2} + 51.2^\circ, t=0) = -2.94 \times 10^3 \text{ V}$$

Assume $\omega_0 \gg \omega = 377 \text{ rad/s}$

$$t = 0$$

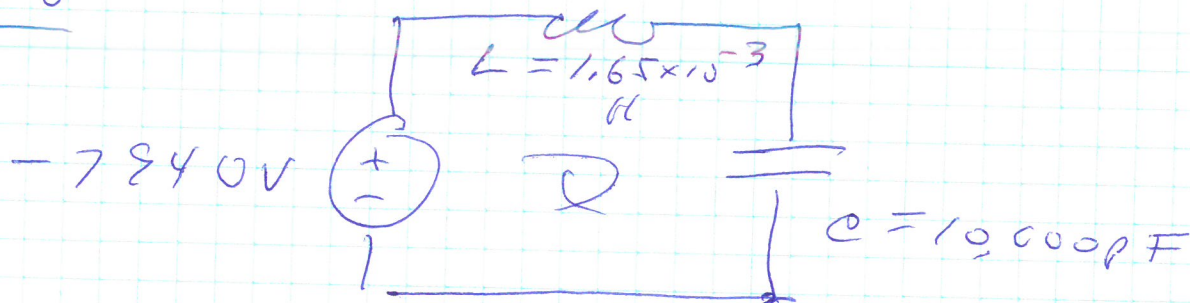

$$\text{At } t=0 \quad i_L(0) = 0 ; \quad v_C(0) = 0$$

$$\text{KVL} \quad L \frac{di}{dt} + v_C = V_S ; \quad i = C \frac{dv_C}{dt}$$

$$\frac{1}{LC} \left(L C \frac{d^2 v_C}{dt^2} + v_C = V_S \right)$$

$$\frac{d^2 v_C}{dt^2} + \frac{1}{LC} v_C = \frac{1}{LC} V_S$$

$$v_{ss}(t) = V_S$$

$$\frac{d^2 v_C}{dt^2} + \frac{1}{LC} v_C = 0 \Rightarrow \text{CHAR EQN}$$

$$s^2 + \frac{1}{LC} = 0$$

$$v_{C_{tr}}(t) = A_1 \cos \omega_s t + A_2 \sin \omega_s t$$

$$s_1, s_2 = \pm j \omega_c$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$v_C(t) = V_S + A_1 \cos \omega_s t + A_2 \sin \omega_s t$$

$$v_C(0) = 0 = V_S + A_1 \Rightarrow A_1 = -V_S$$

$$\frac{dv_C(0)}{dt} = \frac{i(0)}{C} = 0 = 0 - A_1 \omega_s \sin(0) + A_2 \omega_s \cos(0)$$

$$A_2 = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 2.46 \times 10^5 \text{ RAD/SEC}$$

$$(\sim 40 \text{ kHz})$$

$$v_o(t) = -7840 \left[1 - \cos\left(\frac{2.46 \times 10^5 t}{\pi}\right) \right] \quad t \geq 0$$

$$\left| \frac{V_{\text{PEAK}}}{\text{STRESS}} \right| = 2 \times 7840 \approx 15.9 \text{ kV}$$

$$\frac{X}{R_s} = 6 \quad Z_{\text{BASE}} = 6.22 \Omega$$

$$|Z| = \sqrt{R^2 + X^2} = 0.1 \times 6.22 = 0.622 \Omega$$

$$X = 6R \quad 0.622 = \sqrt{R^2 + (6R)^2} = \sqrt{37} R_s$$

$$R_s = \frac{0.622}{\sqrt{37}} = 0.102 \Omega \Rightarrow X = 6R = 0.613 \Omega$$

$$\tilde{I}_f = \frac{\tilde{V}_s}{(R_f + R_s) + j\omega L} = \frac{12.47/\sqrt{3}}{(0.1 + 0.102) + j0.613} = 8.37 \angle \theta - 45.5^\circ \text{ KA}$$


$$v_s(t) = \frac{\sqrt{2} \cdot 12.470}{\sqrt{3}} \cos(377t + \theta)$$

$$i_f(t) = \sqrt{2} \cdot 8.374 \cos(377t + \theta - 45.5^\circ)$$

$$\text{For } i_f(t=0) = 0 \Rightarrow \theta - 45.5^\circ = \frac{\pi}{2}; \quad \theta = \frac{\pi}{2} + 45.5^\circ$$

$$v_s\left(\frac{\pi}{2} + 45.5^\circ\right) = -7262 \text{ V}$$

For $t=0$

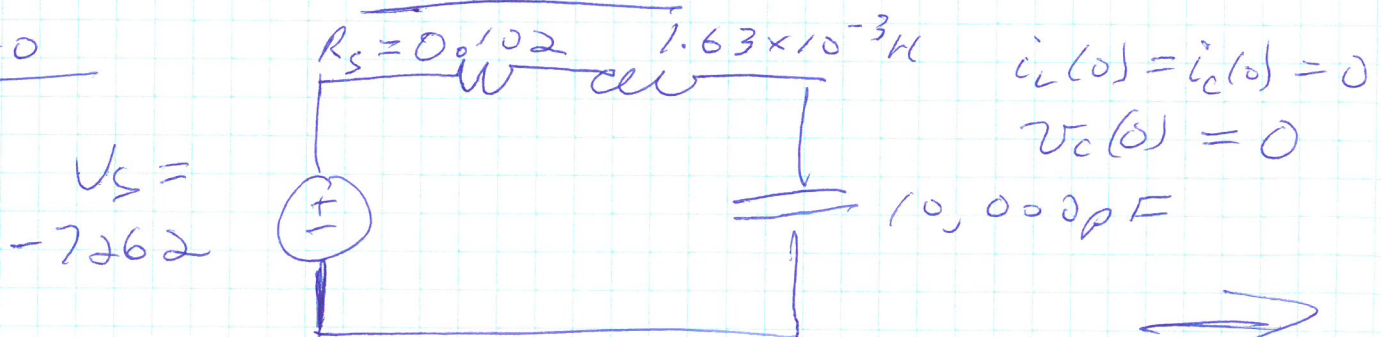

KVL $L \frac{di}{dt} + R i + v_c = V_s ; \dot{i} = C \frac{dv_c}{dt}$

$$L C \frac{d^2 v_c}{dt^2} + R C \frac{dv_c}{dt} + v_c = V_s$$

$$\left/ \frac{d^2 v_c}{dt^2} + \frac{R}{L} \frac{dv_c}{dt} + \frac{1}{LC} v_c = \frac{V_s}{LC} \right/$$

$$v_{ss}(t) = K \Rightarrow \frac{d^2 K}{dt^2} + \frac{R}{L} \frac{dK}{dt} + \frac{1}{LC} K = \frac{V_s}{LC}$$

$$K = V_s \Rightarrow v_{ss}(t) = V_s = -7262$$

CHAR. EQN $s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \Rightarrow b = \frac{R}{L}, c = \frac{1}{LC}$

$$s_1, s_2 = \frac{-b}{2a} \pm \frac{\sqrt{b^2 - 4ac}}{2a} = -31.4 \pm j 2.48 \times 10^5$$

$$v_{c,tn}(t) = e^{-31.4t} [A_1 \cos(2.48 \times 10^5 t) + A_2 \sin(2.48 \times 10^5 t)]$$

$$v_c(t) = -7262 + e^{-31.4t} [A_1 \cos(2.48 \times 10^5 t) + A_2 \sin(2.48 \times 10^5 t)]$$

APPLY BOUNDARY CONDITIONS

$$v_c(0) = 0 = -7262 + e^{(0)} [A_1 \cos(0) + A_2 \sin(0)]$$

$$A_1 = 7262$$

APPLY CHAIN RULE $\frac{d}{dt} [f(t) g(t)] = \frac{df(t)}{dt} g(t) + f(t) \frac{dg(t)}{dt}$

$$\frac{dv_c(0)}{dt} = \frac{\dot{i}(0)}{C} = 0 = 0 - 31.4 e^{(0)} [A_1 \cos(0) + A_2 \sin(0)] + e^{(0)} [-A_1 \omega \sin(0) + A_2 \omega \cos(0)]$$

$$\Rightarrow A_2 = \frac{31.4 A_1}{\omega} = \frac{31.4 (7262)}{2.48 \times 10^5} = \frac{0.9204}{\text{SMALL}}$$

$$v_c(t) = -7262 + e^{-31.4t} \left[7262 \cos(2.48 \times 10^5 t) + 0.9204 \sin(2.48 \times 10^5 t) \right] \approx 0$$

LOOK AT $2.48 \times 10^5 t = \pi$
 $t = 1.2674 \times 10^{-5}$

$$v_{c, \text{PEAK}} \approx -7262 + e^{-31.4(1.2674 \times 10^{-5})} [7262(-1)]$$

$$\approx 2(-7262) = 0.9996 \text{ NOT MUCH ATTENUATION!}$$

$$\approx -14.52$$

SOMEWHAT CLOSE TO WHAT WE SEE IN ~~OUR~~ PLECS SIMULATION

SO ADDING RESISTANCE DID DROP

PEAK STRESS FROM 15.9 \rightarrow 14.5 KV,

BUT NOT A HUGE REDUCTION.

MOSTLY THIS WAS DUE TO SOURCE VOLTAGE AT FAULT CLEARING TIME BEING LOWER IN MAGNITUDE AS OPPOSED TO EXPONENTIAL DAMPING IN SOLUTION.