

## Worked Example


---

Figure below shows a reactor being disconnected from its 7.2 kV supply. During the process of opening, the circuit breaker chops a current of 1.0 A.


Determine

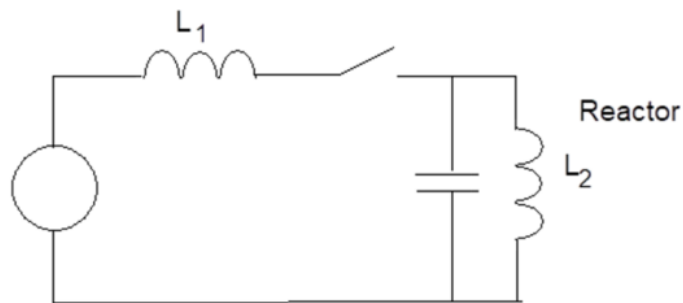- (a) The peak voltage which will appear across the reactor
- (b) Sketch the reactor voltage, the reactor current and the source voltage as a function of time.
- (c) Rework with a 10,000 Ohms equivalent resistance in parallel with reactor.

$$L_1 = 35 \text{ mH}, L_2 = 350 \text{ mH}, C = 3200 \text{ pF}$$



## CURRENT CHOPPING EXAMPLE

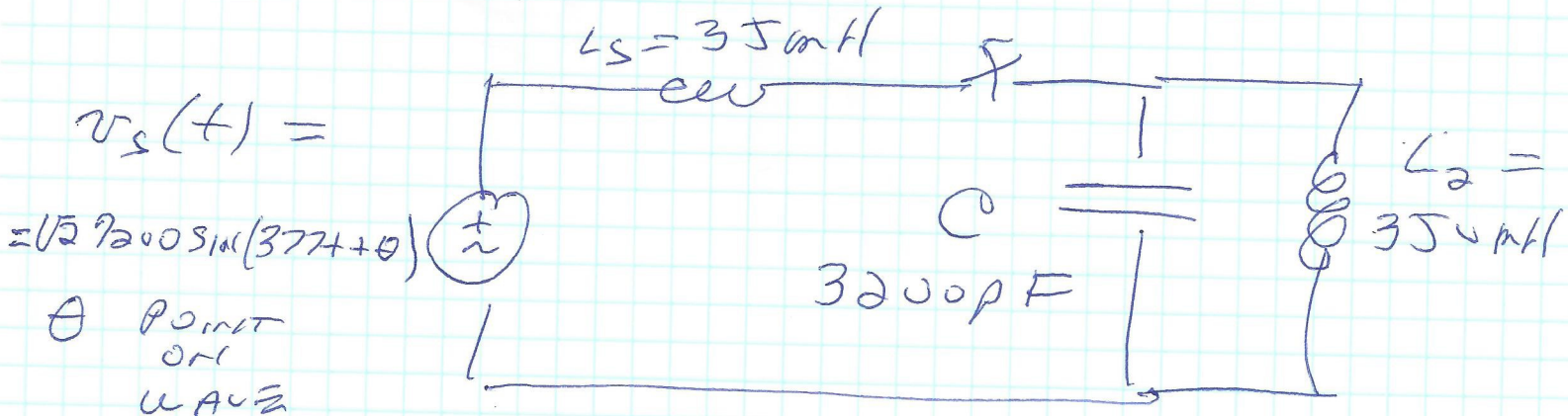12.47 kV 3 $\phi$  circuit, Inductive LOA.LOOK AT CURRENT CHOP OF 1 A FOR  
A CB OPENING

Find PEAK VOLTAGE

$$\omega L_2 = 377 (350 \mu\text{H}) = 131.85 \Omega$$

$$\frac{1}{\omega C} = \frac{1}{377 (3200 \times 10^{-12})} = 828,912 \Omega$$

 $\omega L_2 \ll \frac{1}{\omega C}$  FOR INITIAL CONDITIONS,  
NEGLECT CAPACITOR CURRENT

BEFORE SWITCHING  $\frac{1}{I} = \frac{Z}{V} = \frac{7200 \angle \theta}{j 377 (0.035 + 0.35)} = 49.6 (\theta - 90^\circ)$

$$i(t) = \frac{\sqrt{2} 49.6}{70.15} \sin(377t + \theta - 90^\circ)$$

$$i(t=0) = 0 = \frac{70.15}{70.15} \sin(\theta - 90^\circ)$$

$$\theta_1 = \sin^{-1}\left(\frac{1}{70.15}\right) + 90^\circ$$

$$\theta_2 = 180^\circ - \theta_1$$

$$(\theta_2 - 90^\circ) = 180^\circ - (\theta_1 - 90^\circ)$$


$$\theta_1 = 90.82^\circ$$


$$\theta_2 = 269.18^\circ$$

$$(-90.82^\circ)$$


$$i = \frac{\sqrt{2} 7200 \angle \theta}{j \omega L_s + j \omega L_2}$$
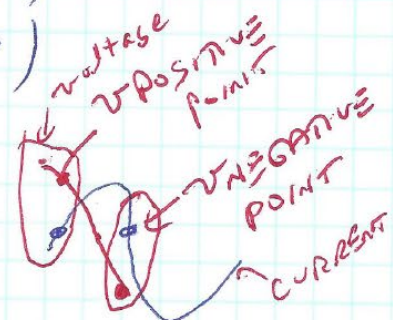
$$v(t) = \frac{350}{385} \sqrt{2} 7200 \sin(\omega t + \theta)$$



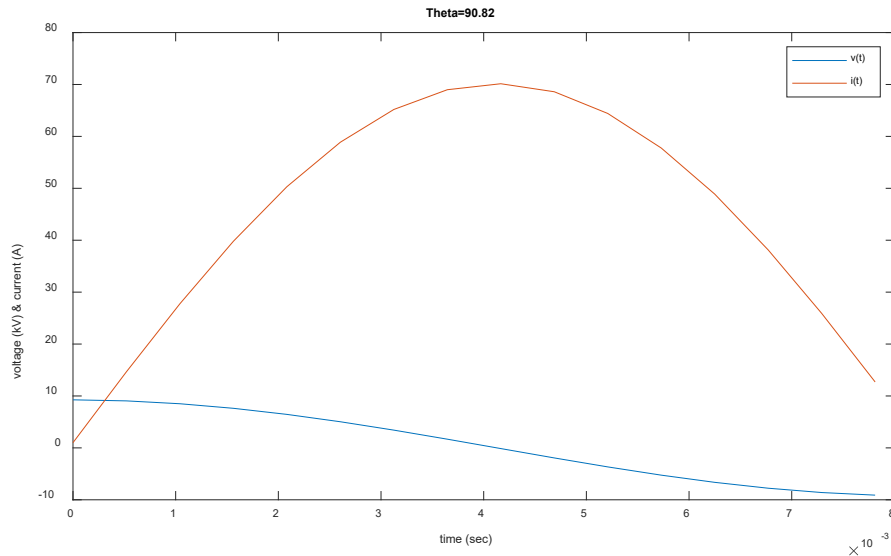

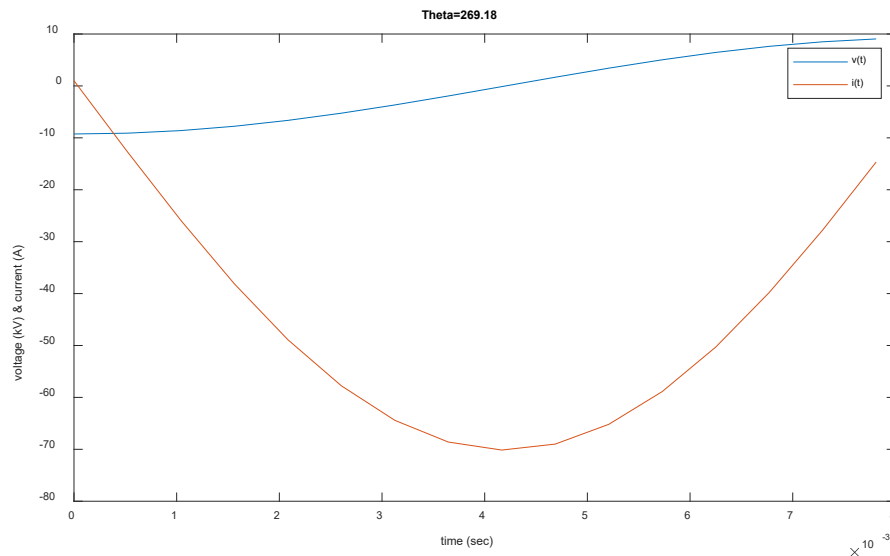For  $\Theta = 90.82$  deg, note that at  $t=0$ , current is 1 A, but increasing. So can't have a current chop condition here, since current is not approaching a natural current zero. Note since current lags voltage by 90 degrees, this corresponds to positive voltage.



For  $\Theta = 269.18$  deg, note at  $t=0$  that current is 1 A, but decreasing. So have the condition where we can have a current chop before the natural current zero. This corresponds to a negative voltage.



# CURRENT PROBLEM EXAMPLE

$$v_c(0) = \frac{350}{385} \sqrt{2} 200 \sin(-89.82^\circ)$$

$$= -9256 \text{ V}$$

-90.82  
CHOOSE ANGLE SO  
VOLTAGE IS NEGATIVE

$$v_c(0) = -9256; i_c(0) = 1.0 \text{ A}; i_c(0) = -1.0 \text{ A}$$

$$\frac{1}{C} \frac{d}{dt} \left( C \frac{dv_c}{dt} + \frac{1}{L} \int v_c dt + i_c(0) \right) = 0$$

$$\frac{d^2 v_c}{dt^2} + \frac{1}{LC} v_c = 0$$

$$s_1, s_2 = \pm j \frac{1}{\sqrt{LC}} \Rightarrow \omega_0 = \frac{1}{\sqrt{0.350 \times 3200 \times 10^{-12}}}$$

$$= 29,881 \text{ RAD/SEC}$$

$$\sim 5 \text{ kHz}$$

$$v_c(t) = A_1 \cos \omega_0 t + A_2 \sin \omega_0 t$$

$$v_c(0) = A_1 \Rightarrow A_1 = -9256$$

$$\frac{dv_c(0)}{dt} = \frac{1}{C} i_c(0) = \frac{1}{C} (-I_0) = \omega_0 A_2$$

$$A_2 = \frac{1}{C} (-I_0) / \omega_0 = -10,958$$

$$v_c(t) = -9256 \cos(29,881t) - 10,958 \sin(29,881t)$$

$$= 13,986 \cos(29,881t + 131.40^\circ) \quad t \geq 0$$

# CURRENT CHOPPING EXAMPLE

1/9/1/20/1

A) 10,000  $\Omega$  RESISTANCE IN PARALLEL TO REPRESENT DAMPING

$\omega L_2 = 131.95$ , DO WE NEED TO INCLUDE FOR INITIAL CONDITIONS

NO  $R \rightarrow Z_{LOAD} = j131.95 = 131.95 \angle 90^\circ$

WITH  $R \Rightarrow Z_{LOAD} = \frac{R(j\omega L)}{R + j\omega L} = 131.94 \angle 89.2^\circ$

AS FAR AS ANGULAR DIF.  $\sin(89.2) \approx 1$  } NOT MUCH DIF. SO CAN NEGLECT SINCE COMPONENT TOLERANCE  $> 1\%$

SO NEGLECTING  $R$  IN INITIAL CONDITIONS

GIVES US  $v_c(0) = -9256 = v_c(0); i_L(0) = -1A$

AFTER SWITCHING, APPLY KCL

$$\frac{1}{C} \frac{d}{dt} \left( C \frac{dv_c}{dt} + \frac{1}{L} \int_0^t v_c dt + i_L(0) + \frac{v_c}{R} \right) = 0$$

$$\frac{d^2 v_c}{dt^2} + \frac{1}{RC} \frac{dv_c}{dt} + \frac{1}{LC} v_c = 0$$

$$s_1, s_2 = \frac{-1/RC \pm \sqrt{(1/RC)^2 - \frac{4}{LC}}}{2} = -15,625 \pm j25,470$$

$$v_c(t) = e^{-15,625t} (A_1 \cos(25,470t) + A_2 \sin(25,470t)) \quad (4kHz)$$

$$v_c(0) = -9256 = e^{(0)} (A_1(1) + A_2(0)); A_1 = -9256$$

$$\frac{dv_c(0)}{dt} = \frac{1}{C} \left( \underbrace{-i_L(0) - i_R(0)}_{-1} \right) = \frac{1}{C} \left( -1.9256 - \frac{-9256}{10,000} \right) = -3.125 \times 10^8$$



$$\frac{dv_c(t)}{dt} = -15,625 e^0 (A_1(1) + A_2(0)) + e^0 (A_1 25470(0) + A_2 25470 \cos(0))$$

$$\Rightarrow A_2 = \frac{-3.125 \times 10^8 + 15625(A_1)}{25,470}$$

$$= -17,948$$

$$v_c(t) = e^{-15,625t} (-9256 \cos(25,470t) - 17,948 \sin(25,470t))$$

$$= e^{-15,625t} [20,194 \cos(25,470t + 117.3^\circ)]$$

$$\text{WHEN } 25,470t + 117.3^\circ = \pi \Rightarrow t_m = 4.296 \times 10^{-5}$$

$$e^{-15625t_m} (-20,194) = -10,320 \text{ V}$$

BUT

-12.3 k IN SIMULATION

NEED TO PLOT

FROM PLOT -12.3 kV

