


Worked Example 1

A surge with the characteristics shown travels down an overhead line towards a cable that has a resistive termination. The circuit, illustrated below, has the following characteristics:

O/H line	$Z_o = 300 \text{ Ohms}$	velocity = 980 ft/microsec. (0.298704 km/microsec)
Cable	$Z_o = 50 \text{ Ohms}$	velocity = 400 ft/microsec. (0.12192 km/microsec)
Load	$Z = 200 \text{ Ohms}$	


Calculate:

- (a) Plot the voltage at the 200 Ohm load resistor, Point 2, as a function of time for a time period of 10 microseconds after the disturbance hits the junction between the overhead and underground cable.
- (b) Plot the voltage at the junction of the overhead and underground cable, point 1, as a function of time for a time period of 10 microseconds after the disturbance hits the junction between the overhead and underground cable.
- (c) Verify the results in (a) and (b) using an EMTP simulation. Include your code and plots of the voltage at Point 1 and Point 2.

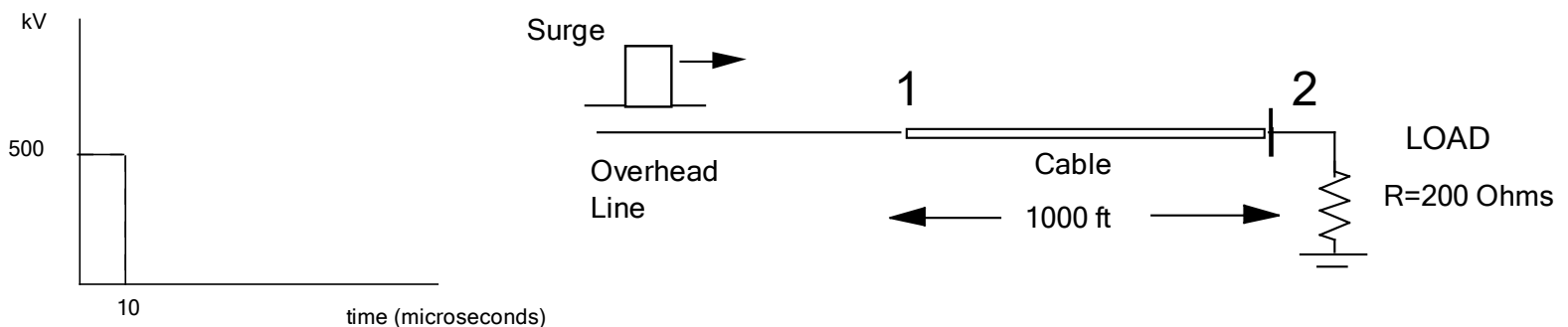

ECSE 557
FALL 2019

EXAMPLE 1 - SQUARE WAVE 9/25/19 1/2

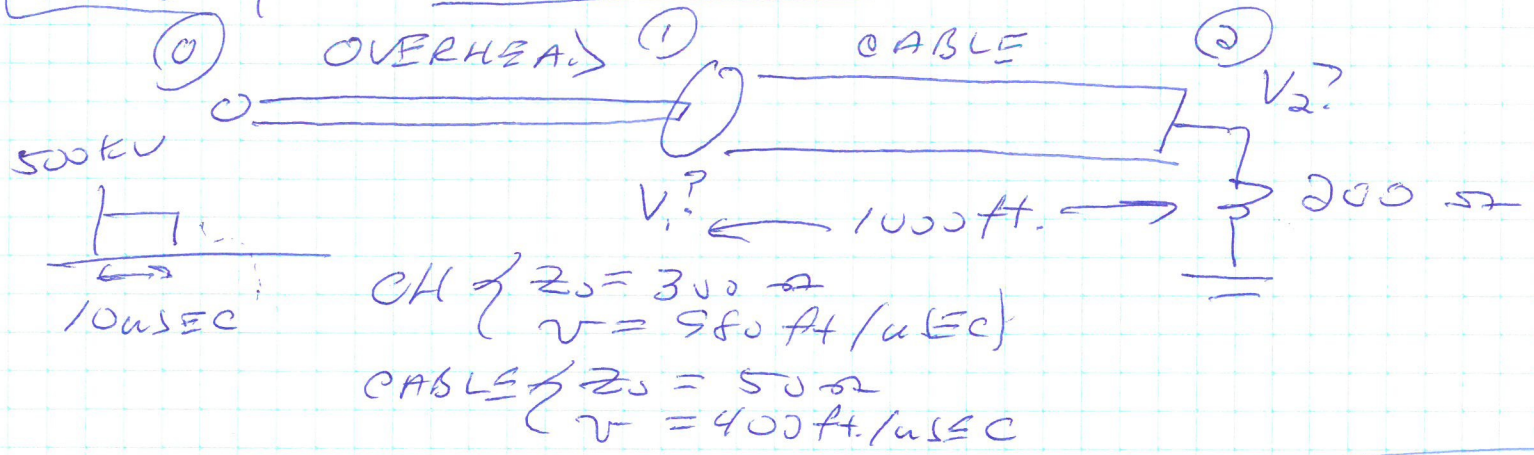

$$\tau_{\text{CABLE}} = \frac{l}{v} = \frac{1000 \text{ ft}}{400 \text{ ft}/\mu\text{sec}} = 2.5 \mu\text{sec}$$


REFRACTION AT ① $\Gamma_{b1} = \frac{2Z_B}{Z_A + Z_B} = \frac{2(50)}{300 + 50} = \underline{0.286}$

REFLECTION AT ② $\Gamma_{a2} = \frac{Z_B - Z_A}{Z_B + Z_A} = \frac{200 - 50}{200 + 50} = \underline{0.6}$


REFLECTION AT ① $\Gamma_{a1} = \frac{Z_B - Z_A}{Z_B + Z_A} = \frac{300 - 50}{300 + 50} = \underline{0.714}$

EXAMPLE 1 - SQUARE WAVE


2/2

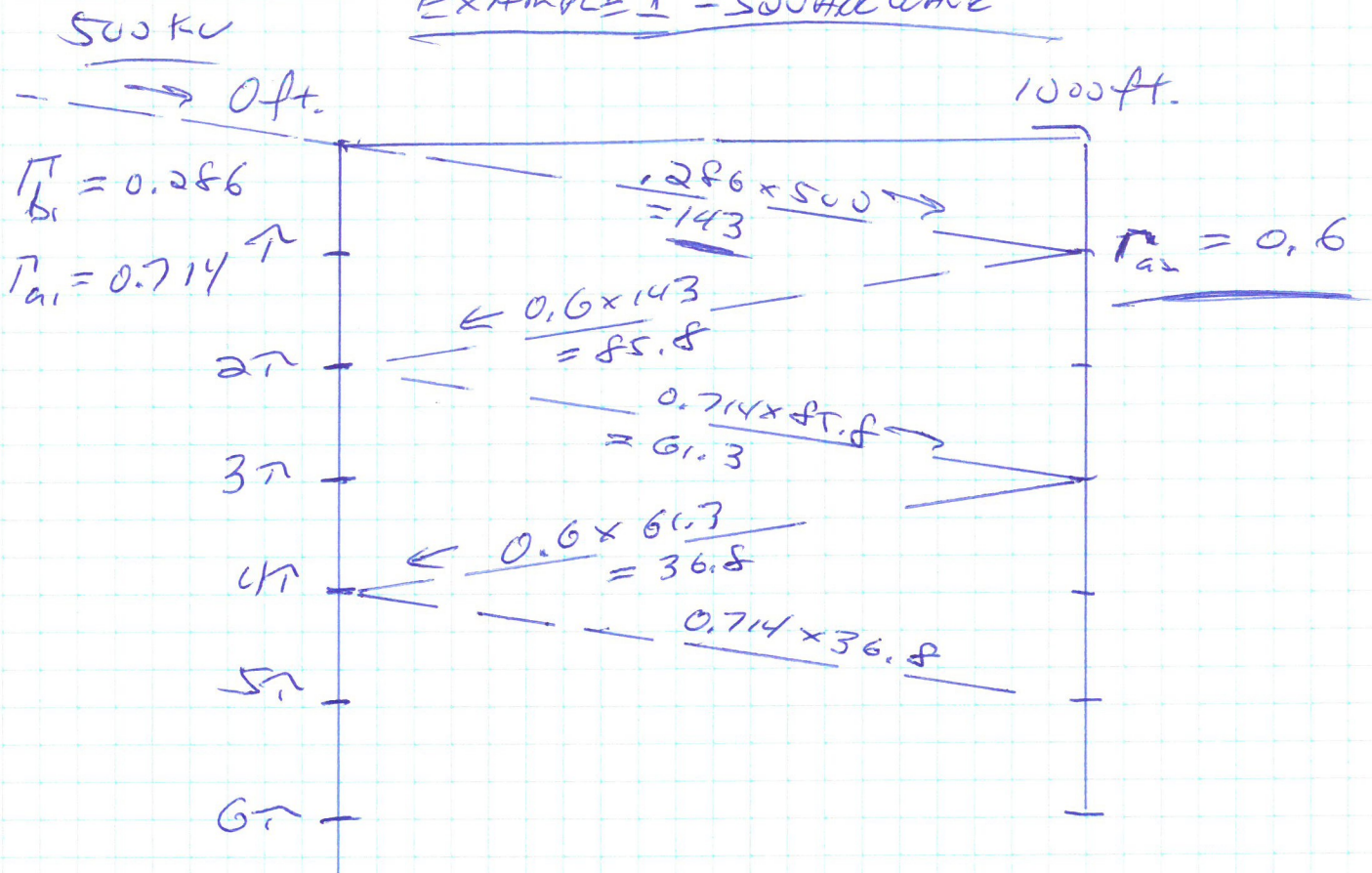

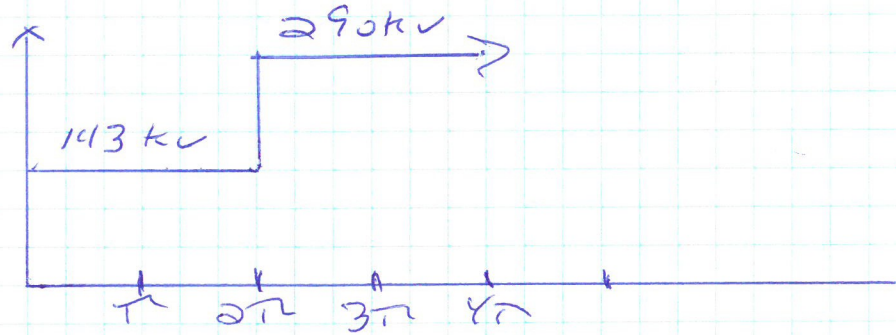SENDING END OF CABLE ($t=0$ WHEN SURGE HITS CABLE)



RECEIVING END OF CABLE

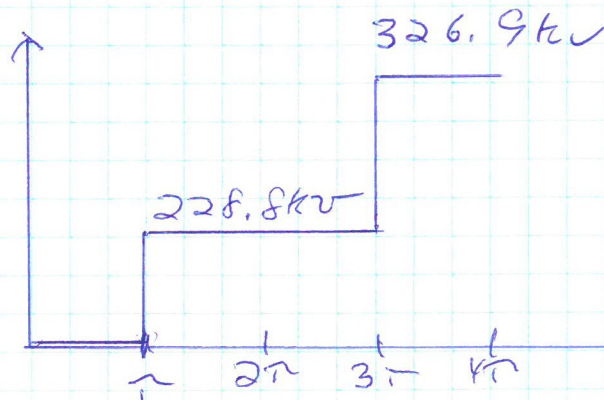


Worked Example 2

The single-phase 12.47kV (line-to-line) circuit shown below is energized at the peak of the voltage cycle. The remote end is connected to a 500 Ohm load. The pre-insertion resistor has a value of 300 Ohms. The cables have the following characteristics:

O/H line	$Z_o = 300 \text{ Ohms}$	velocity = 980 ft/microsec. (0.298704 km/microsec)
Cable	$Z_o = 50 \text{ Ohms}$	velocity = 490 ft/microsec. (0.149352 km/microsec)

Assuming that the source can be modeled as a constant DC voltage source:

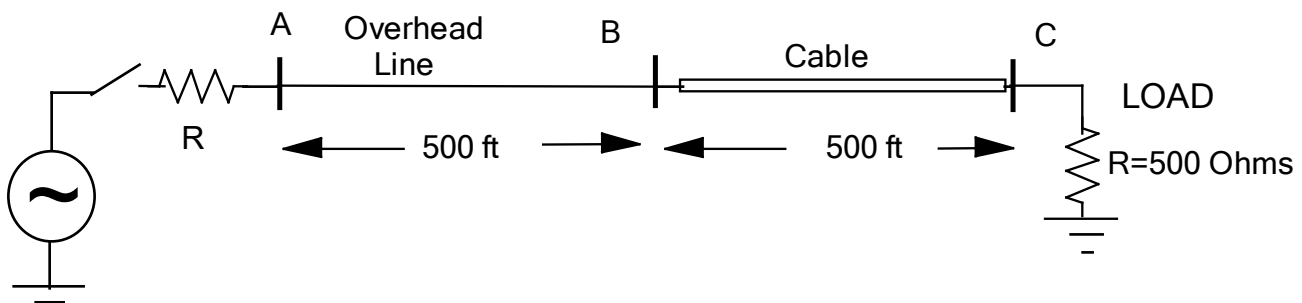- (a) Plot the voltage at the 500 Ohm load resistor, Point C, as a function of time for a time period of 3.0 microseconds after the switching operation occurs. Make sure to include numerical values for the amplitude levels and transition times.
- (b) Plot the voltage at the junction of the overhead and underground cable, point B, as a function of time for a time period of 3.0 microseconds after the switching operation occurs.




1-2-1
ONE

$$\Gamma_b = \frac{2(300)}{350} = 1.71 \quad \Gamma_a = \frac{300-50}{350} = .71$$

$$\Gamma_a = \frac{50-300}{350} = -.71 \quad \Gamma_b = \frac{2(50)}{350} = .29$$

10
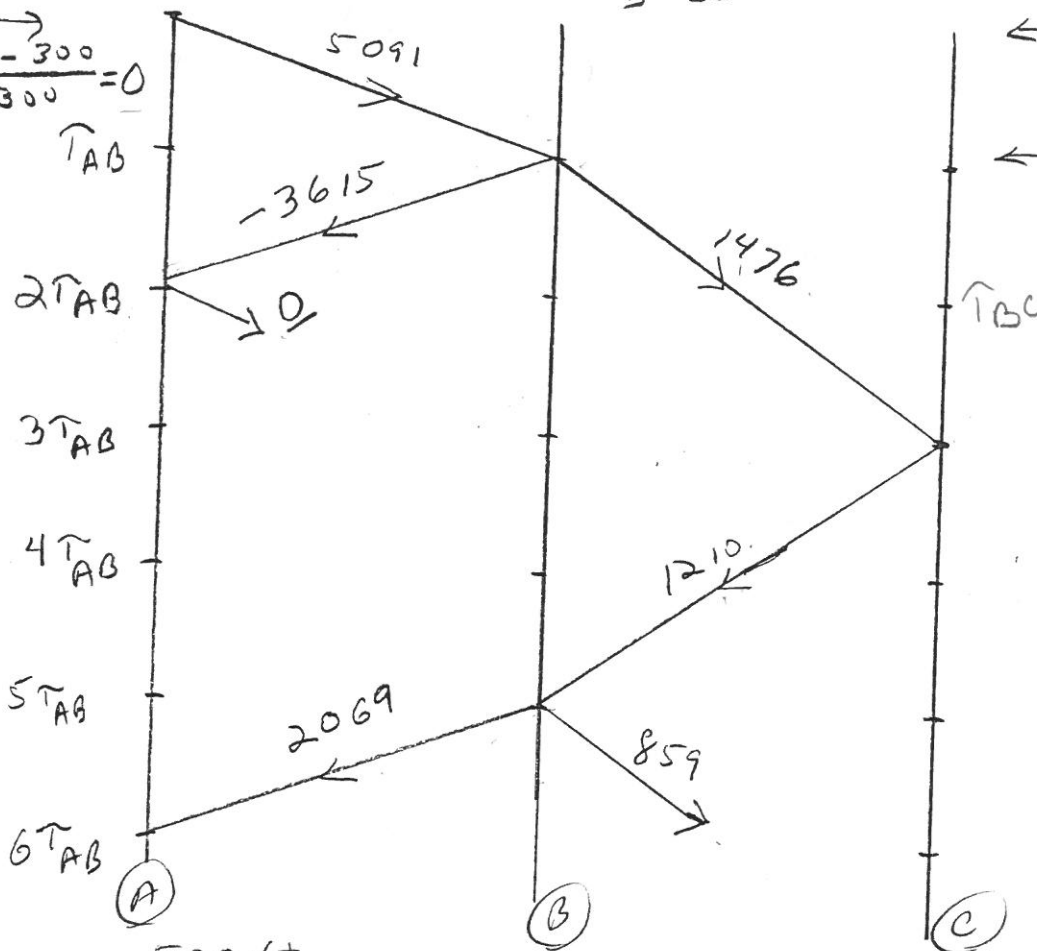
$$\Gamma_a = \frac{300-300}{300+300} = 0$$



$$\Gamma_a = \frac{500-50}{500+50} = .82$$

$$\Gamma_b = \frac{2(500)}{500+50} = 1.82$$

$$\tau_{AB} = \frac{500 \text{ ft.}}{980 \text{ ft./}\mu\text{sec}} = .51 \mu\text{sec} \quad \tau_{BC} = \frac{500}{490 \text{ ft./}\mu\text{sec}} = 1.02 \mu\text{sec.}$$

$$V_{SRC} = \frac{\sqrt{2}}{\sqrt{3}} 12.47 \times 10^3 = 10,182 \text{ V}$$

$$V_{FNT} = \frac{300}{300+300} 10,182 = 5091 \text{ V}$$

Ex 2

2.)

ONE

